

①  
Assignment Network Theory  
TEMPLECITY INSTITUTE OF TECHNOLOGY & ENGINEERING (TITE)


Writing Space

CHAPTER-1

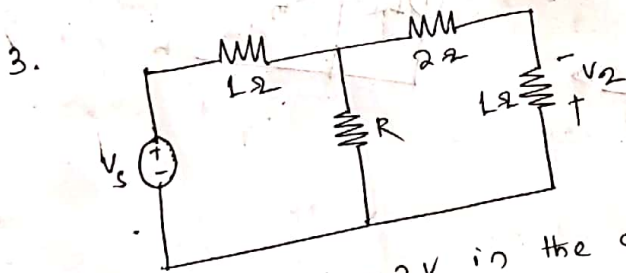- Q1. Write down the definitions and unit
- Magnetizing force
  - flux
  - Intensity.
2. Relationship between flux, flux density and magnetizing force.
3. What is self inductance and mutual inductance?


CHAPTER-II

- Write down the procedure for solving a circuit by Node Analysis.
- Write down the procedure for solve a circuit by Mesh Analysis.



Given  $I_1 = 1A$ ,  $V_2 = 2V$  in the circuit shown in fig, the  $V_s$  is given by \_\_\_\_\_.

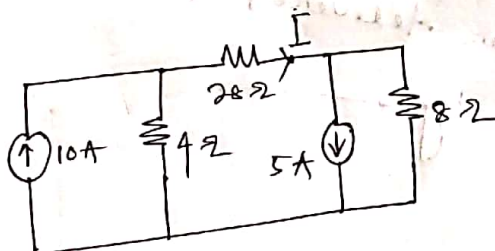4. In the circuit of fig, the current  $I$  will be \_\_\_\_\_.



①  
 TEMPLE CITY INSTITUTE OF TECHNOLOGY & ENGINEERING (TITE)  
 Network Theory  
CHAPTER - III  
 Writing space




1. Write down the statements

- Thevenin's Theorem
- Norton's Theorem.


2. What is Maximum power Transfer Theorem.

UNIT - IV

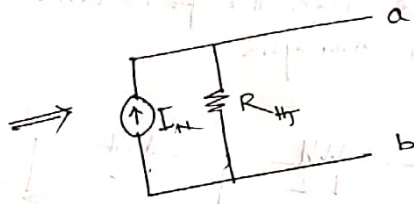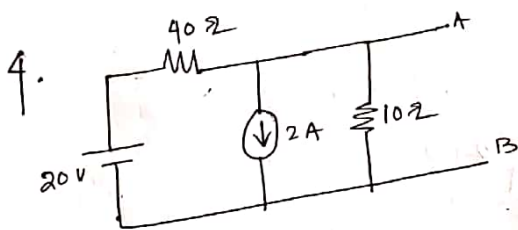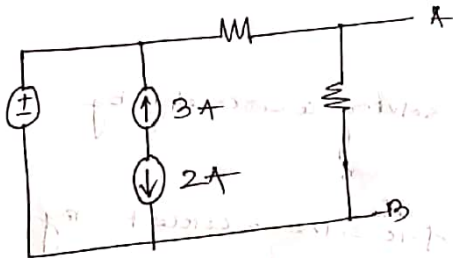3. The Thevenin's equivalent across the terminals 'AB' in the fig. is.




Find  $I_N$  &  $R_{Th}$ .

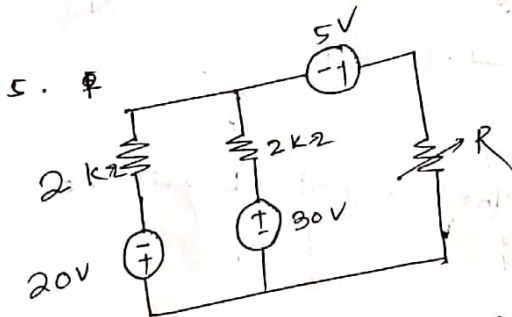


Find the Maximum power delivered to the load. Resistor 'R' is given by \_\_\_\_\_.

CHAPTER - IV

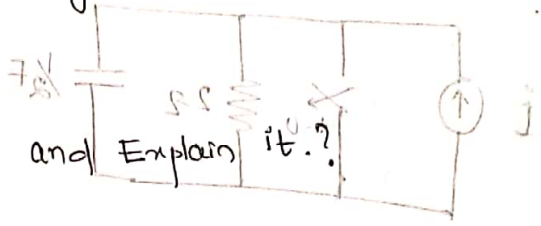What is power factor, power angle, RMS and peak value.



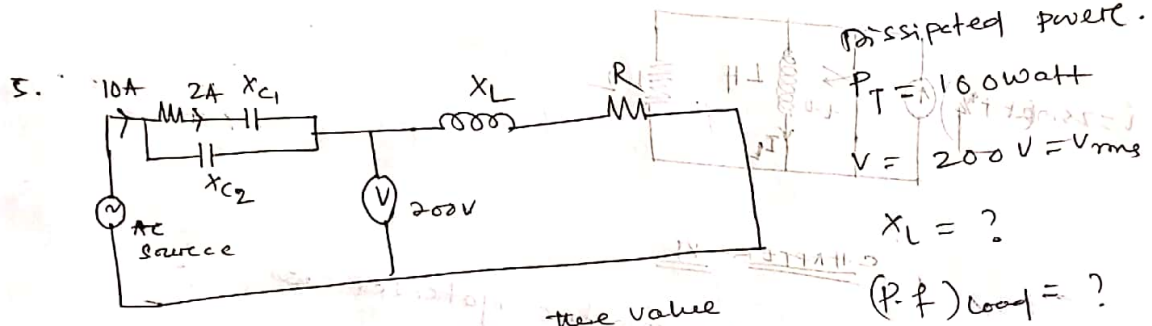
- What is power Triangle and Explain it.?
- What is Resonant frequency, Bandwidth, Q-factor in series circuit
- Relationship between phase and line quantities in star & delta connection.



\* In this circuit all these value are RMS values.


- $V(t) = -170 \sin(\omega t - \pi/6)$  Volt  
 $I(t) = 8 \cos(\omega t + \pi/6)$  A  
 Find  $P_{avg}$ ?

CHAPTER - V

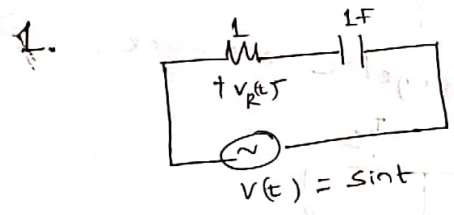


steady state voltage  $v_L(t)$  is

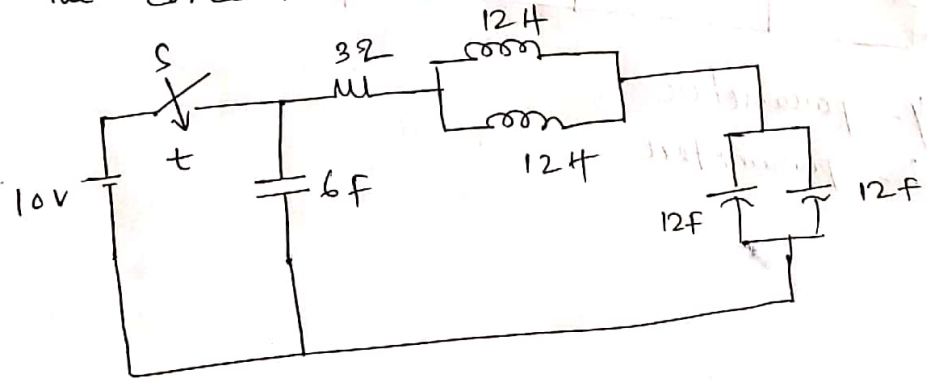- Consider the figure and Find Time constant of the circuit




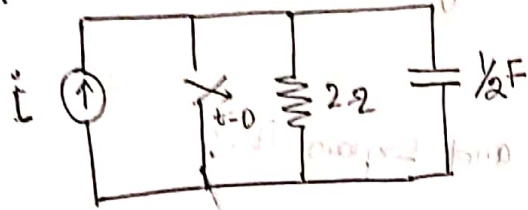3. In the circuit shown in figure, the steady state voltage across the resistor is \_\_\_\_\_



$$i = 2 \cos(t + \pi/4)$$

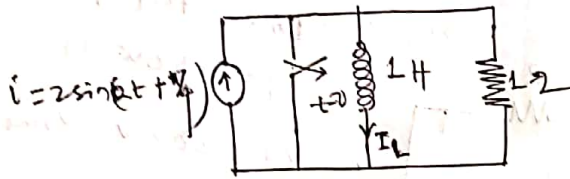4. In the circuit shown in the figure, the steady state current through Inductor  $I_L$  is \_\_\_\_\_




CHAPTER - VI

1. Note down the parameter matrices.

- i. Z-parameter
- ii. Y-parameter
- iii. Transmission parameter
- iv. Hybrid parameter
- v. g-parameter.

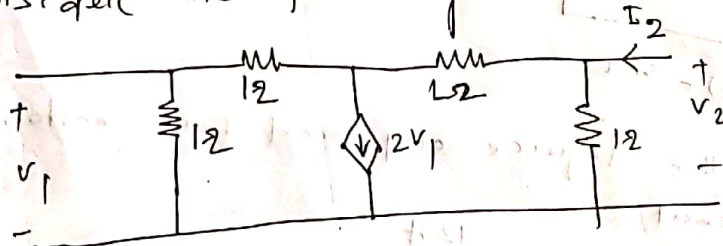2. Consider the following parameter Network.




- a. y-parameter
- b. h-parameter



Writing Space

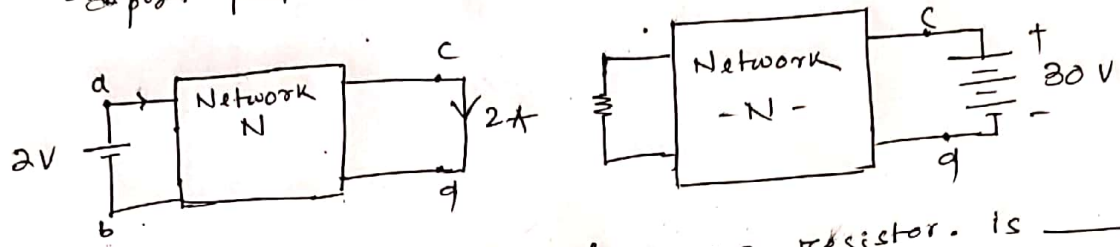
Q. 3. Two sets of measurements of a linear passive two-port network are shown in the following fig.



Current flowing through the 2Ω resistor is \_\_\_\_\_

CHAPTER - VII

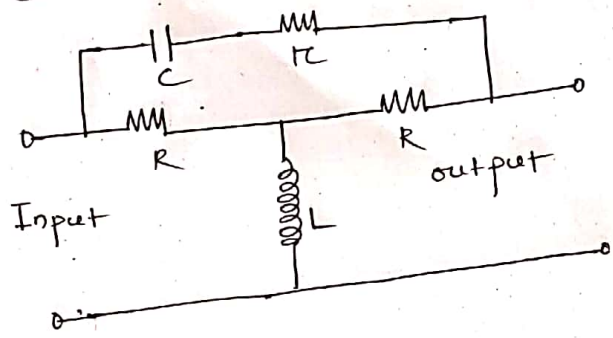1. The circuit shown in the fig. is a \_\_\_\_\_



2. Match the List  
List - I

- a.  $H(s) = \frac{100}{(s^2 + 50s + 100)}$
- b.  $H(s) = \frac{100}{(s^2 + 50s + 100)}$
- c.  $H(s) = (1-s)/(1+s)$
- d.  $H(s) = \frac{s^2 + 100}{(s^2 + 50s + 100)}$

List - II

- 1. LPF
- 2. HPF
- 3. BPF
- 4. BSF
- 5. All pass filter

3.  $H(s) = \frac{s^2 - 5 + 1}{s^2 + 2s + 1}$  represent a ~~filter~~ filter.

- a) LPF                      c) HPF
- b) BPF                      d) BSF